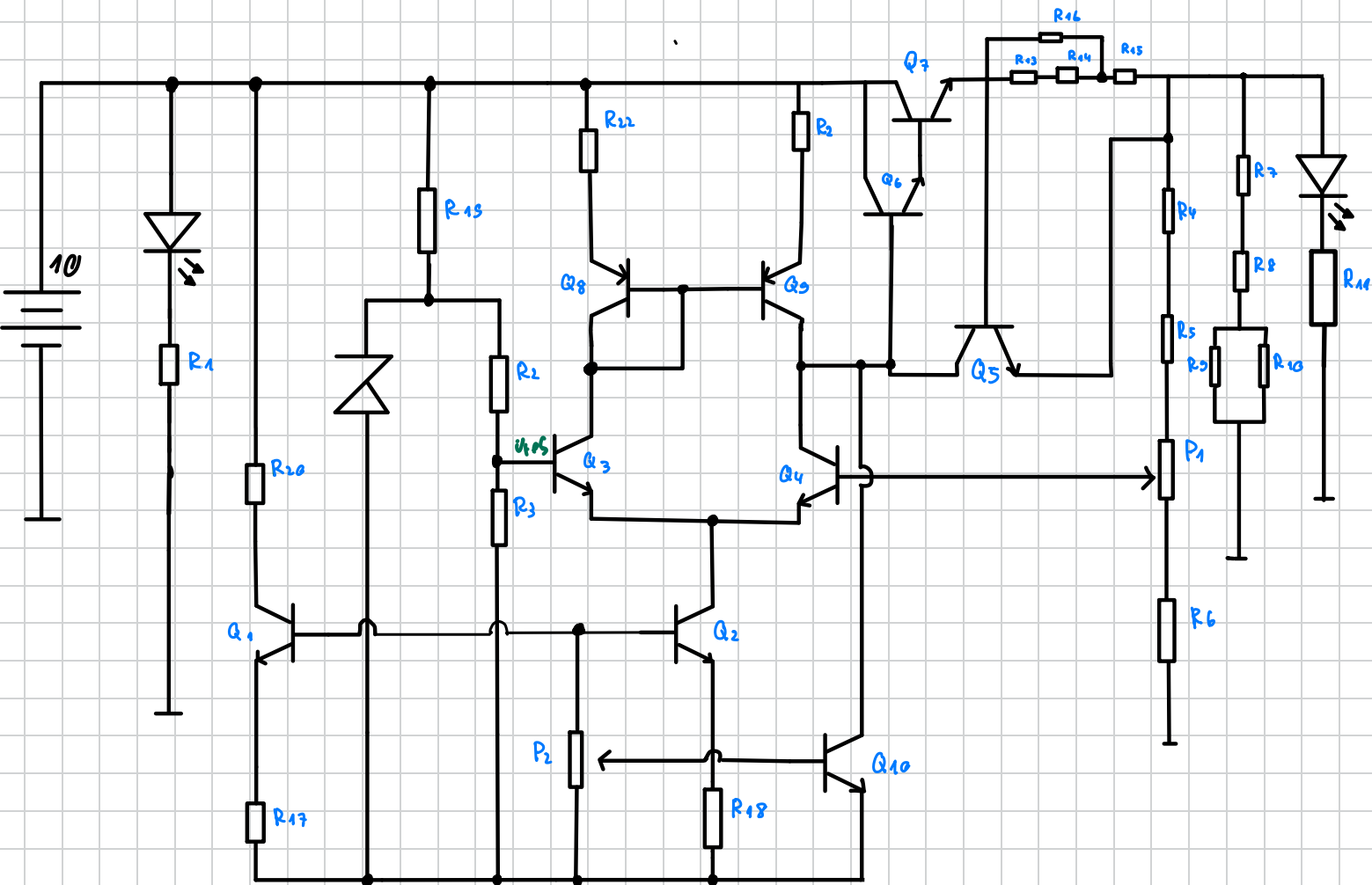


# Calcularea punctului static de Funcționare



$$R_1 = 1k\Omega$$

$$R_6 = 3.9k\Omega$$

$$R_{11} = 220\Omega$$

$$R_{17} = 220\Omega$$

$$R_2 = 3.3k\Omega$$

$$R_7 = 100\Omega$$

$$R_{13} = 1\Omega$$

$$R_{18} = 220\Omega$$

$$R_3 = 3.3k\Omega$$

$$R_8 = 100\Omega$$

$$R_{14} = 1\Omega$$

$$R_{19} = 1k\Omega$$

$$R_4 = 5.6k\Omega$$

$$R_9 = 100\Omega$$

$$R_{15} = 1\Omega$$

$$R_{20} = 5.6k\Omega$$

$$R_5 = 680\Omega$$

$$R_{10} = 100\Omega$$

$$P_1 = 5k\Omega$$

$$P_2 = 5k\Omega$$

$$R_{21} = 100\Omega$$

$$R_{22} = 100\Omega$$

$$R_{16} = 1\Omega$$

$$Q_3 + Q_4 - \text{etaj diferentia} \Rightarrow V_{inm} = V_{inp}$$

$$V_{inm} = V_{tes} = V_{D1} \cdot \frac{R_3}{R_2 + R_3} = 2,7 \cdot \frac{1}{2} = 1,35 \text{ V}$$

$$I_{C8} = I_{C9} = I_{C3} = I_{C4} = \frac{I_{C5}}{2} = \frac{I_{C1}}{2}$$

$$I_{C9} = \frac{V_1 - V_{BE9}}{R_{20} + R_{17}} = \frac{10 - 0,7}{5,820 \cdot 10^3} \approx 1,6 \text{ mA}$$

$$\Rightarrow I_{C8} = 1,6 \text{ mA}$$

$$I_{C5} = 1,6 \text{ mA}$$

$$I_{C3} = 1,6 \text{ mA}$$

$$I_{C4} = 1,6 \text{ mA}$$

$$I_{C5} = 3,2 \text{ mA}$$

$$I_{C1} = 3,2 \text{ mA}$$

$$V_{CE9max} = V_{omin} + V_{BE7} + V_{BE6} - V_{R21} - V_{CE4} - V_{CE2} - V_{R18}$$

$$V_{CE5} = V_{tes} - V_{BE3} - V_{R18} \cdot I_{C2} = 1,35 - 0,7 - 0,3 = 0,35 \text{ V}$$

$$V_{CE1} = V_{1max} - I_{C8} \cdot R_{22} - I_{C1} \cdot R_{18} = 10 - 0,08 - 0,7 - 0,45 - 0,3 = 8,47 \text{ V}$$

$$V_{CE2max} = V_{omax} + V_{BE7} + V_{BE6} - V_{CE2} - V_{R18} = 5 + 0,7 - 0,45 - 0,3 = 5,45 \text{ V}$$

$$V_{CE2min} = V_{CE2max} \mid V_{omin} = 2,5 \text{ V}$$

$$V_{CE5max} = 2,5 + 1,4 - 0,08 - 0,55 - 0,45 - 0,3 = 2,32 \text{ V}$$

$$V_{CE1} = 2,8 \text{ V}$$

$$I_{LEDmax} = 15 \text{ mA}$$

$$R_{LEDout} = \frac{V_{omax} - V_{LED}}{I_{LED}} = \frac{5 - 2,8}{15 \cdot 10^{-3}} = 147 \Omega$$

$$R_{LEDin} = \frac{V_{1max} - V_{LED}}{I_{LED}} = \frac{10 - 2,8}{15 \cdot 10^{-3}} = 480 \Omega$$

## Potenci na rezistorima

$$P_{R1} = I_{R1}^2 \cdot R_1 = 10^3 \cdot (7 \cdot 10^{-3})^2 = 49 \cdot 10^{-3} = 49 \text{ mW}$$

$$P_{R2} = I_{R2}^2 \cdot R_2 = 3,3 \cdot 10^3 \cdot (1450 \cdot 10^{-4})^2 = 3,3 \cdot 10^3 \cdot 202500 \cdot 10^{-16} = 600 \mu\text{W}$$

$$P_{R3} = I_{R3}^2 \cdot R_3 = 3,3 \cdot 10^3 \cdot (439 \cdot 10^{-4})^2 = 613 \mu\text{A}$$

$$P_{R4} = I_{R4}^2 \cdot R_4 = 5,6 \cdot 10^3 \cdot (165 \cdot 10^{-4})^2 = 5,6 \cdot 10^3 \cdot 165^2 \cdot 10^{-16} = 1,52 \cdot 10^{-4} = 1,52 \text{ mW} = 152 \mu\text{W}$$

$$P_{R5} = I_{R5}^2 \cdot R_5 = 680 \cdot (165 \cdot 10^{-4})^2 = 680 \cdot 10^{-4} \cdot 165^2 = 1,85 \cdot 10^{-5} = 18,5 \cdot 10^{-6} = 18,5 \mu\text{W}$$

$$P_{R6} = I_{R6}^2 \cdot R_6 = 3,3 \cdot 10^3 \cdot (165 \cdot 10^{-4})^2 = 3,3 \cdot 10^3 \cdot 165^2 \cdot 10^{-16} = 0,106 \text{ mW} = 106 \mu\text{W}$$

$$P_{R7} = I_{R7}^2 \cdot R_7 = 100 \cdot (10 \cdot 10^{-3})^2 = 100 \cdot 10^{-2} \cdot 10^{-6} = 10 \text{ mW}$$

$$P_{R8} = I_{R8}^2 \cdot R_8 = 100 \cdot (10 \cdot 10^{-3})^2 = 100 \cdot 10^{-2} \cdot 10^{-6} = 10 \text{ mW}$$

$$P_{R9} = I_{R9}^2 \cdot R_9 = 100 \cdot (5 \cdot 10^{-3})^2 = 100 \cdot 25 \cdot 10^{-6} = 2,5 \text{ mW}$$

$$P_{R10} = I_{R10}^2 \cdot R_{10} = 100 \cdot (5 \cdot 10^{-3})^2 = 100 \cdot 25 \cdot 10^{-6} = 2,5 \text{ mW}$$

$$P_{R11} = I_{R11}^2 \cdot R_{11} = 220 \cdot (120 \cdot 10^{-3})^2 = 220 \cdot 400 \cdot 10^{-6} = 88 \text{ mW}$$

$$P_{R13} = I_{R13}^2 \cdot R_{13} = 1 \cdot (10 \cdot 10^{-3})^2 = 10 \mu\text{W}$$

$$P_{R14} = I_{R14}^2 \cdot R_{14} = 1 \cdot (10 \cdot 10^{-3})^2 = 10 \mu\text{W}$$

$$P_{R15} = I_{R15}^2 \cdot R_{15} = 1 \cdot (10 \cdot 10^{-3})^2 = 10 \mu\text{W}$$

$$P_{R16} = I_{R16}^2 \cdot R_{16} = 1 \cdot (7 \cdot 10^{-3})^2 = 49 \mu\text{W}$$

$$P_{R17} = I_{R17}^2 \cdot R_{17} = 220 \cdot (1,5 \cdot 10^{-3})^2 = 220 \cdot 1,5 \cdot 1,5 \cdot 10^{-6} = 450 \mu\text{W}$$

$$P_{R18} = I_{R18}^2 \cdot R_{18} = 220 \cdot (1,5 \cdot 10^{-3})^2 = 220 \cdot 1,5 \cdot 1,5 \cdot 10^{-6} = 495 \mu W$$

$$P_{R19} = I_{R19}^2 \cdot R_{19} = 10^3 \cdot (7,5 \cdot 10^{-3})^2 = 10^3 \cdot 10^{-6} \cdot 7,5 \cdot 7,5 = 56,25 \text{ mW}$$

$$P_{R20} = I_{R20}^2 \cdot R_{20} = 5,6 \cdot 10^3 \cdot (2 \cdot 10^{-4})^2 = 5,6 \cdot 10^3 \cdot 4 \cdot 10^{-8} = 224 \text{ mW}$$

$$P_{R21} = I_{R21}^2 \cdot R_{21} = 1000 \cdot (0,93 \cdot 10^{-3})^2 = 993 \cdot 0,93 \cdot 10^{-6} \cdot 10^2 = 0,96 \cdot 10^{-4} = 96 \mu W$$

$$P_{R22} = I_{R22}^2 \cdot R_{22} = 1000 \cdot (0,96 \cdot 10^{-3})^2 = 998 \cdot 0,96 \cdot 10^{-6} \cdot 10^2 = 0,92 \cdot 10^{-4} = 92 \mu W$$

## Puteriile pe tranzistori

$$P_{Q1} = I_{C1} \cdot V_{CE1} = 1,5 \cdot 10^{-3} \cdot 8,47 = 12,7 \text{ mW}$$

$$P_{Q2} = I_{C2} \cdot V_{CE2} = 1,5 \cdot 10^{-3} \cdot 5,45 = 8,175 \text{ mW}$$

$$P_{Q3} = I_{C3} \cdot V_{CE3} = 10^{-3} \cdot 8 = 8 \text{ mW}$$

$$P_{Q4} = I_{C4} \cdot V_{CE4} = 0,5 \cdot 10^{-3} \cdot 3 = 1,5 \text{ mW}$$

$$P_{Q5} = I_{C5} \cdot V_{CE5} = 1,5 \cdot 10^{-3} \cdot 0,5 = 750 \mu W$$

$$P_{Q6} = I_{C6} \cdot V_{CE6} = 1,5 \cdot 10^{-6} \cdot 0,6 = 900 \mu W$$

$$P_{Q7} = I_{C7} \cdot V_{CE7} = 10 \cdot 10^{-3} \cdot 8 = 80 \text{ mW}$$

$$P_{Q8} = I_{C8} \cdot V_{CE8} = 10^{-3} \cdot 50 \cdot 10^{-3} = 50 \mu W$$

$$P_{Q9} = I_{C9} \cdot V_{CE9} = 10^{-3} \cdot 34 \cdot 10^{-3} = 34 \mu W$$

$$P_{Q10} = I_{C10} \cdot V_{CE10} = 5 \cdot 10^{-6} \cdot 4 = 20 \mu W$$

## Puttile p.e diode

$$P_{D1} = V_{D1} \cdot I_{D1} = 2,7 \cdot 7,4 \cdot 10^{-3} = 20 \text{ mW}$$

$$P_{D2} = V_{D2} \cdot I_{D2} = 2,8 \cdot 15 \cdot 10^{-3} = 42 \text{ mW}$$

$$P_{D3} = V_{D3} \cdot I_{D3} = 2,8 \cdot 15 \cdot 10^{-3} = 42 \text{ mW}$$

## Deriva térmica

$$V_{BE7} \rightarrow V_{BE4}$$

$$R_{sus} \rightarrow R_1 + R_7 \text{ (Q7-pot)}$$

$$R_{ics} \rightarrow R_{42} + R_2$$

$$\frac{\Delta V_o}{\Delta T} = \frac{\Delta (R_1 + R_7 + R_5 \cdot (V_{BE4} + V_{D1}) \cdot \frac{1}{R_6})}{\Delta T}$$

$$\frac{\Delta V_o}{\Delta T} = \frac{R_1 + R_7 + R_5}{R_4} \cdot \left( \frac{\Delta V_{BE4}}{\Delta T} + \frac{\Delta V_{D1}}{\Delta T} \right)$$

$$\Rightarrow \frac{\Delta V_o}{\Delta T} = \frac{5 \cdot 10^3 + 5,6 \cdot 10^3 + 680}{3,5 \cdot 10^3} \cdot (0,3)$$

$$\Rightarrow \frac{\Delta V_o}{\Delta T} = 0,86 \frac{\text{mV}}{^{\circ}\text{C}}$$